


For HP 5384A frequency counter 10 MHz reference output (-20 dBm, square wave)

Will drive multiple 50Ω loads.

Built from generic Chinese 30 dB, 5 GHz MMIC amplifier board

Power: +15 to 30 V

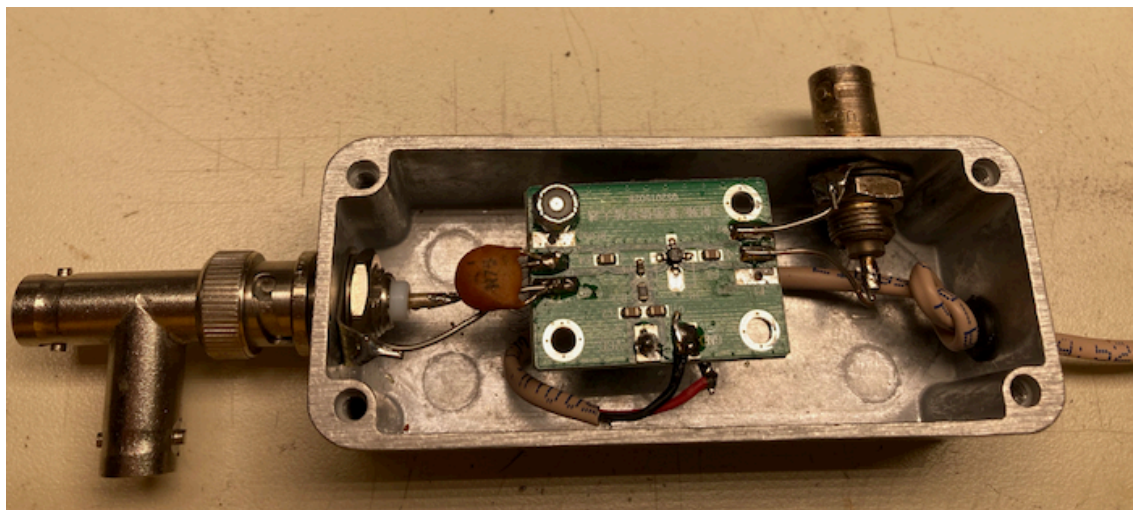Modify HP 5384A by jumpering CR14 with a cliplead. This provides about 17 VDC at the "Ext Pwr" jack.



**10 MHz Distribution Amp**

NA60 9-17-22